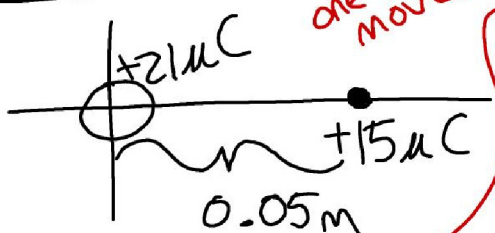


QUIZ P 21



They are fixed moves.


$$W = q(V_A - V_\infty)$$

$$= (15 \times 10^{-9}) \left[\frac{(9 \times 10^9)(21 \times 10^{-9})}{0.05} - 0 \right]$$

$$= 56.7 \text{ J}$$

$$W = \Delta E$$
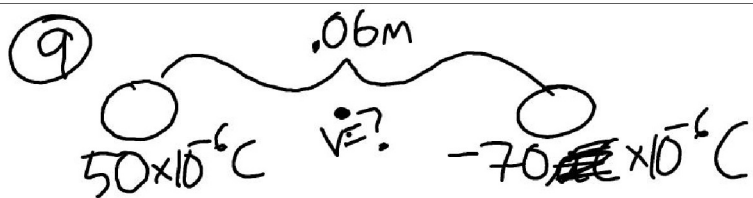
$$W = E_A - E_\infty = \frac{kq_1q_2}{r_A} - \frac{kq_1q_2}{r_\infty} = \frac{(9 \times 10^9)(21 \times 10^{-9})(15 \times 10^{-9})}{0.05} - \frac{(9 \times 10^9)(21 \times 10^{-9})(15 \times 10^{-9})}{\infty}$$




$$V_{\text{net}} = V_1 + V_2$$

$$= \frac{(9 \times 10^9)(50 \times 10^{-6})}{0.03} + \frac{(9 \times 10^9)(-70 \times 10^{-6})}{0.03}$$

$$= -6 \times 10^6 \text{ V}$$


6

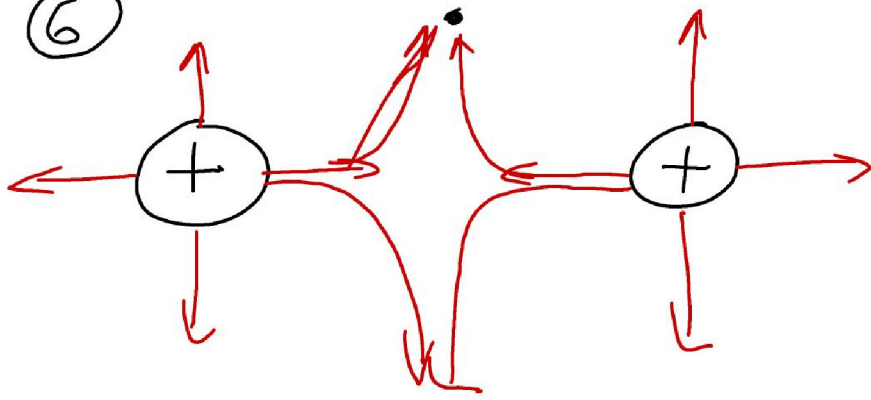

10

$$q = 400 \times 10^{-6} \text{ C}$$
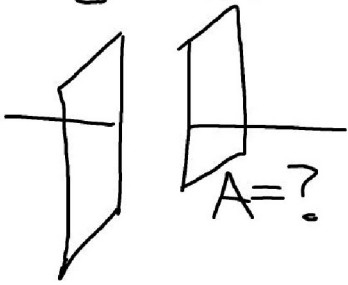
$$E = 4.8 \times 10^8 \frac{\text{N}}{\text{C}}$$



$$\sigma = \frac{q}{A}$$


$$\vec{E} = \frac{\sigma}{\epsilon_0} = \vec{E} = \frac{q}{A\epsilon_0}$$

$$A = \frac{q}{E\epsilon_0}$$

substitute & solve





11

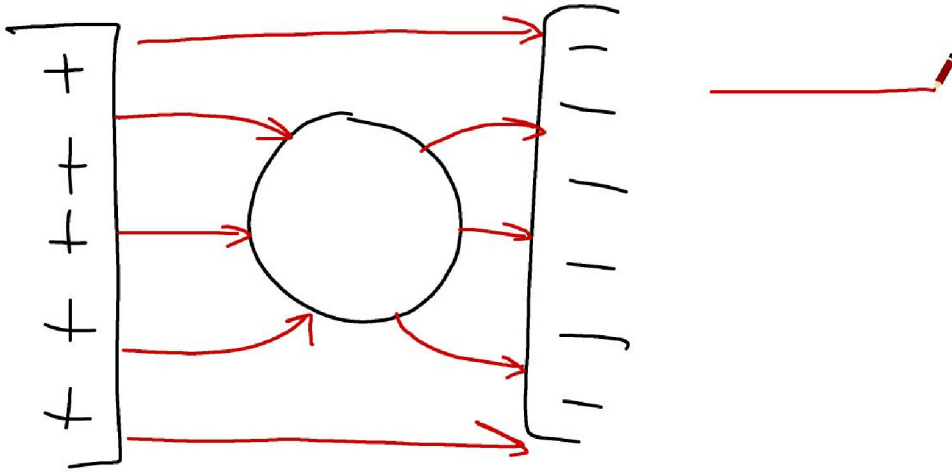




Circuits

Voltage Source (Batteries or generators)

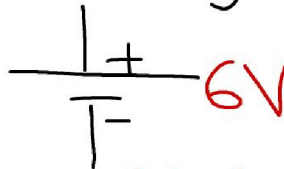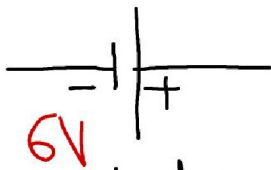

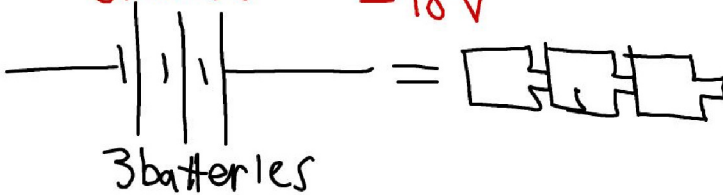connected in series $\rightarrow V_{net} = V_1 + V_2 + V_3$
 $= 18V$



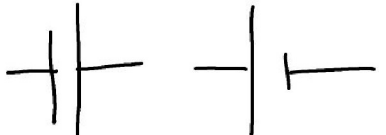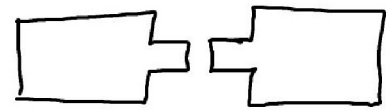

1.5 V

(-1.5V)


b/c it's backward

$$V = 1.5 + (-1.5) \\ = 0V$$



Capacitors

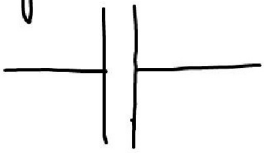store charge, have a voltage drop across
capacitance is measured in ^{then} Farads (F)



$$q = CV$$

charge Capacitance Potential

K = dielectric constant

$$K = \frac{E_0}{E} = \frac{\text{Electric Field w/out dielectric}}{\text{E w/ dielectric}}$$

$$C = \frac{K\epsilon_0 A}{d}$$

distance between plates




Energy stored in a capacitor


$$E = \frac{1}{2} qV = \frac{1}{2} CV^2$$

$$q = CV \quad \frac{1}{2} (CV)V = \frac{1}{2} CV^2$$

Series (in order)

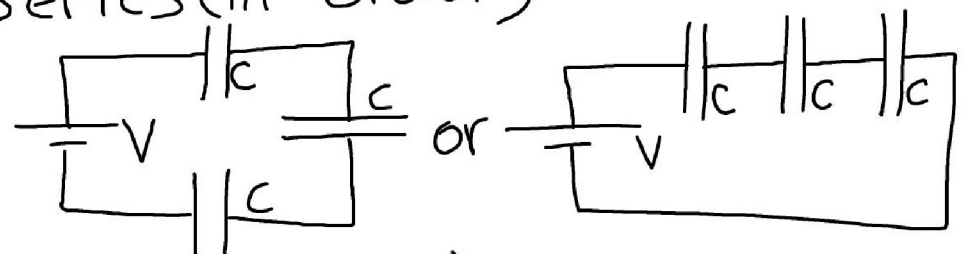

Parallel (next to)

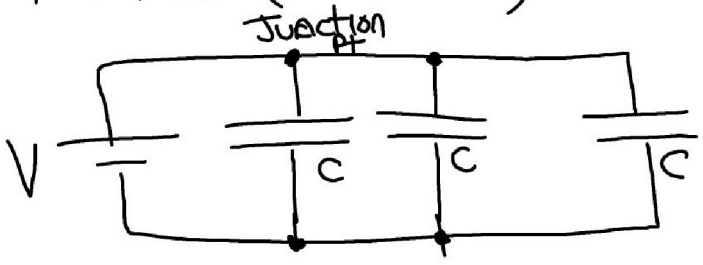

Current - flow of electrons

symbol: I

unit: A = Amperes

$$I = \frac{q}{t}$$

flows from \uparrow
+

Capacitors in...

Series

All have same q

$$\frac{1}{C_{\text{Net}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

sum of V in loop = 0

Parallel

All have same V

$$C_{\text{Net}} = C_1 + C_2 + C_3$$

$$q_{\text{Net}} = q_1 + q_2 + q_3 \dots$$



Resistors

Things that use electric Power
(lightbulbs/heaters)



Symbol for Resistance: R

Unit: Ohm (Ω)



Ohm's Law

$$V = IR$$

Power

$$P = IV$$
$$= I(IR) = I^2R$$

