

598P39)

$$C = 850 \times 10^{-6} \text{ F}$$

$$V = 280 \text{ V}$$

A) Energy

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} (850 \times 10^{-6}) (280 \text{ V})^2$$

$$= 33.32 \text{ J}$$

$$t = 3.9 \times 10^3 \text{ s}$$

$$P = \frac{W}{t} = \frac{\Delta E}{t} = \frac{33.32 \text{ J}}{3.9 \times 10^3 \text{ s}}$$

$$= 8544 \text{ W}$$



29

$$q = 1.5 \times 10^{-8} \text{ C}$$

$$V_1 = 190 \text{ V}$$

$$V_2 = 75 \text{ V}$$


$$r = ?$$

$$V = \frac{kq}{r}$$

$$r = \frac{kq}{V}$$

$$r_1 = \frac{(9 \times 10^9)(1.5 \times 10^{-8})}{190} = 0.71$$
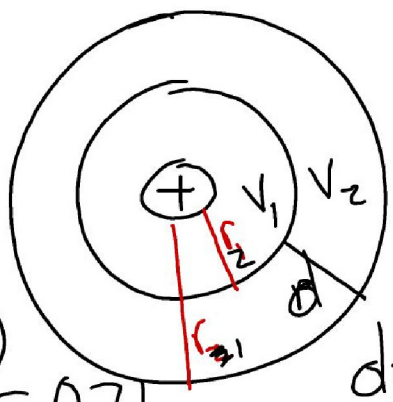
$$r_2 = \frac{(9 \times 10^9)(1.5 \times 10^{-8})}{75} = 1.8$$



$$d = r_2 - r_1$$

$$= 1.09 \text{ m}$$



Resistors

Series

$$R_{\text{net}} = R_1 + R_2 + R_3 + \dots$$
$$\cancel{R_{\text{net}}} = \sum R$$

Voltage "Drops" across a resistor, according to $V = IR$

Current is the same in every resistor



Parallel

$$\frac{1}{R_{\text{net}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Voltage is the same

To get current, use $V = IR$

$$\frac{1}{R_{\text{net}}} = \sum \frac{1}{R_i}$$

Electro Motive Force (EMF) (\mathcal{E})

Treat this like V

$$\mathcal{E} = IR$$

Ammeter - measures current
Ideally: low R_i in Series



Voltmeter - measures potential or EMF



Ohmmeter - Measures Resistance
Ideally: High R_i in Parallel

