

18 WS 152

$120\ \Omega$ & $86\ \Omega$ in parallel

$$R_1 = 120\ \Omega$$

$$R_2 = 86\ \Omega$$

Parallel

want R_{eq}


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{120} + \frac{1}{86}$$

$$\frac{1}{R_{eq}} = \frac{86}{10320} + \frac{120}{10320}$$

$$\frac{1}{R_{eq}} = \frac{206}{10320}$$

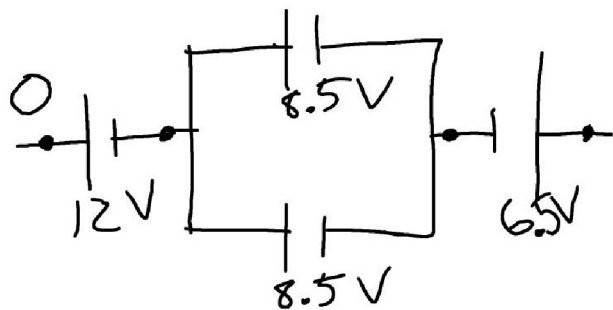
$$R_{eq} = \frac{10320}{206} = 50\ \Omega$$



$$-12V - 8.5V + 6.5V = -14V$$



⑧ NO, Ammeters have a low resistance, in parallel, they steal the current.
(Current determines bulb brightness)

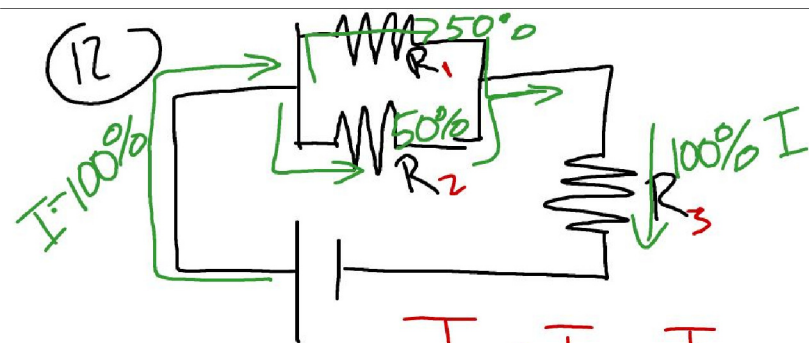⑪ ○ Amps. Voltmeters have high resistance, so the current is blocked!



$$I_1 + I_2 = I_3 \text{ or } I_1 = I_2 = \frac{1}{2} I_3$$

(13)

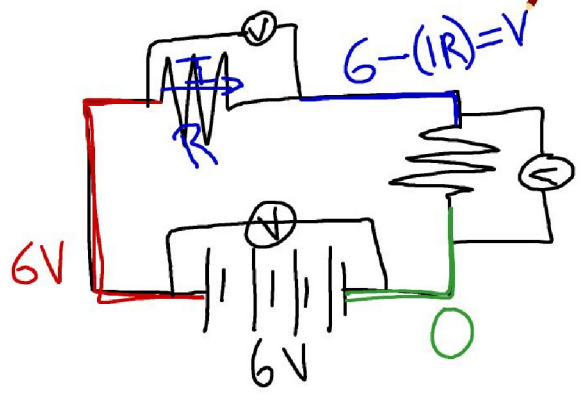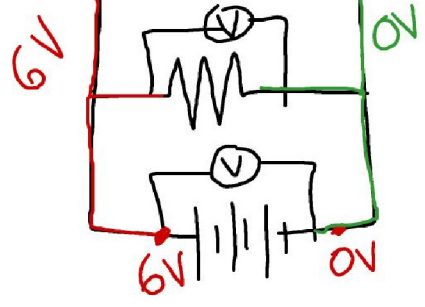

Voltmeter
 ~~$V = IR$~~
 ~~$V = (\infty)(\infty)$~~



Notes

Resistance in wires

$$R = \frac{\rho L}{A}$$

ρ = Resistivity


L = length

A = cross sectional area



Kirchoff's Rules

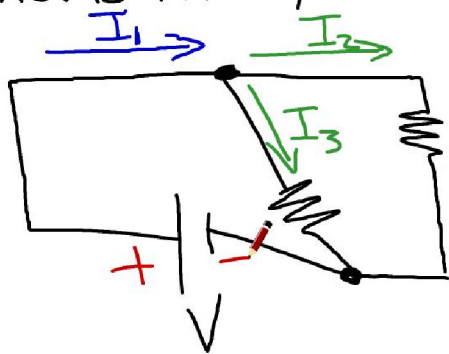
① Junction Rule; current in = current out



$$I_1 = I_2 + I_3$$



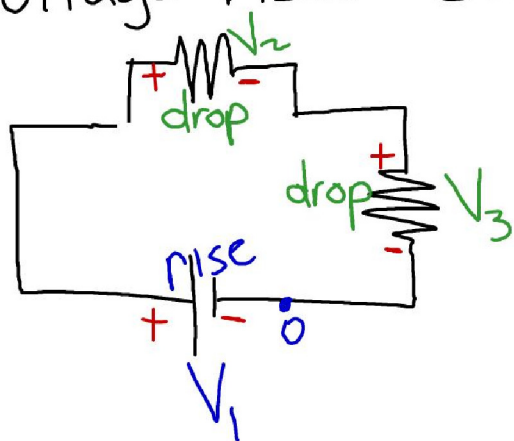Loop Rule : In a closed loop, sum of voltage rises = SUM of voltage drops.



$$|V_1| = |V_2 + V_3|$$

